32 AC Circuits


32.1 AC Sources and Phasors

- 1. The figure shows emf phasors A, B, and C.
 - a. What is the instantaneous value of the emf?

A 60V B-100V C 80V

b. At this instant, is the magnitude of the emf increasing, decreasing, or holding constant?

A Decreasing B Decreasing C Increasing

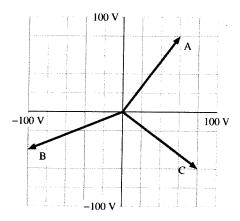



2. Draw a phasor diagram for the following emfs.

a. $(100 \text{ V})\cos \omega t$ at $\omega t = 240^{\circ}$

b. (400 V) $\cos \omega t$ at $t = \frac{1}{3}T$


c. (200 V) $\cos \omega t$ at t = 0

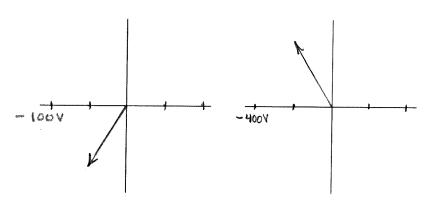

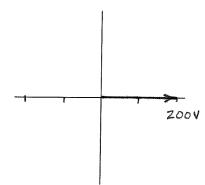

- 3. The current phasor is shown for a 10 Ω resistor.
 - a. What is the instantaneous resistor voltage v_R ?

$$V_R = i_R R = (-4A)(1052) = -40V$$

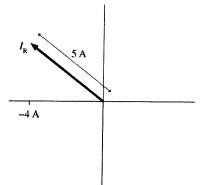

b. What is the peak resistor voltage V_R ?

$$V_{R} = I_{R} R = (5A)(10\Omega) = 50V$$

- 4. A circuit consists of one resistor connected to an emf. The peak current through the resistor is 4.0 A. What is the peak current if:
 - a. The resistance R is doubled?

$$2.0A$$
 $I_R = \frac{V_R}{R}$

b. The peak emf \mathcal{E}_0 is doubled?

8.0A
$$I_R = \frac{V_R}{R} = \frac{\mathcal{E}_0}{R}$$

c. The frequency ω is doubled?

32.2 Capacitor Circuits

- 5. A circuit consists of one capacitor connected to an emf. The peak current through the capacitor is 4.0 A. What is the peak current if:
 - a. The peak emf \mathcal{E}_0 is doubled?

8.0A
$$I_c = \omega C V_c = \omega C E_o$$


b. The capacitance C is doubled?


c. The frequency ω is doubled?

- 6. Current and voltage graphs are shown for a capacitor circuit with $\omega = 1000$ rad/s.
 - a. What is the capacitive reactance $X_{\rm C}$?

$$X_c = \frac{V_c}{T_c} = \frac{10V}{0.01A} = 1000\Omega$$

b. What is the capacitance C?

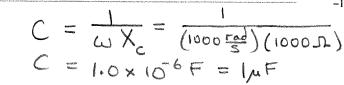


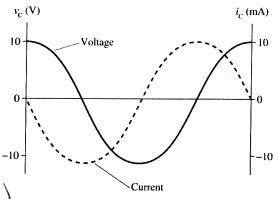

7. A 13 μ F capacitor is connected to a 5.5 V/250 Hz oscillator. What is the instantaneous capacitor current i_C when $\mathcal{E}=-5.5$ V?

Zero. When $\mathcal{E}=-\mathcal{E}_0$, the voltage phasor angle is 180°. The current phasor leads the voltage phasor by 90° so it is at 270° which gives $i_{\rm C}=0$ since $\cos(270^\circ)=0$.

8. Consider these three circuits.

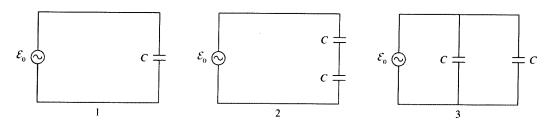


Rank in order, from largest to smallest, the peak currents $(I_C)_1$ to $(I_C)_3$ provided by the emf.

Order:
$$(I_c)_3 > (I_c)_1 > (I_c)_2$$

Explanation:
$$I_c = \omega C V_c$$

$$C_1 = C \qquad C_2 = \frac{1}{2} C \qquad C_3 = 2C$$

9. Consider these four circuits.

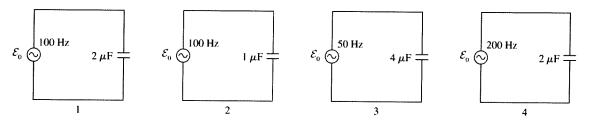

Rank in order, from largest to smallest, the capacitive reactances $(X_C)_1$ to $(X_C)_4$.

Order:
$$(X_c)_2 > (X_c)_1 = (X_c)_3 > (X_c)_4$$

Explanation:
 $X_c = \frac{1}{\omega C} = \frac{1}{2\pi f C}$ so $X_c \propto \frac{1}{f C}$
Smaller values of fC give larger X_c .
 $f_1C_1 = (100H_2)(2\mu F) = 200\mu F/s$
 $f_2C_2 = 100\mu F/s$ $f_3C_3 = 200\mu F/s$ $f_4C_4 = 4100\mu F/s$

32.3 RC Filter Circuits

- 10. A low-pass RC filter has a crossover frequency $f_c = 200$ Hz. What is f_c if:
 - a. The resistance R is halved?

$$f_c = 400 \, \text{Hz}$$
 since $f_c = \frac{1}{2\pi} \left(\frac{1}{RC} \right)$.

b. The capacitance C is halved?

c. The peak emf \mathcal{E}_0 is halved?

11. What new resistor value R will give this circuit the same value of ω_c if the capacitor value is changed to:

a.
$$C = 1 \mu F$$


b.
$$C = 4 \mu F$$

c.
$$C = 20 \,\mu\text{F}$$


$$R = 400 \Omega$$


$$R = 100 - \Omega$$


$$R = 20 \Omega$$

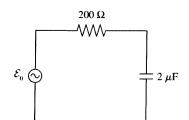

12. Consider these three circuits.

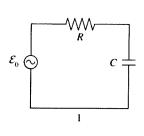

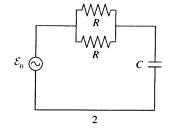

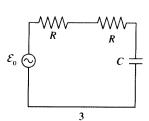

Rank in order, from largest to smallest, the crossover frequencies ω_{c1} to ω_{c3} .

WCZ > WCI > WCZ Order: Explanation:

$$O_{C_1} = \frac{1}{RC}$$

$$\omega_{c_1} = \frac{1}{Rc}$$
 $\omega_{c_2} = \frac{1}{(\frac{R}{2})c} = 2\omega_{c_1}$

$$\omega_{c3} = \frac{1}{(2R)C} = \frac{1}{2} \omega_{c1}$$

13. The text claims that $V_R = V_C = \mathcal{E}_0/\sqrt{2}$ at $\omega = \omega_c$. If this is true, then $V_R + V_C > \mathcal{E}_0$. Is it possible for their sum to be larger than \mathcal{E}_0 ? Explain.

Yes. In fact, VR+Vc is always larger than Eo in an RC circuit (where both R and C are nonzero). VR and Vc are two sides of a right triangle with Eo as the hypotenuse (E2=VR+V2). Also, the peak voltages do not

32.4 Inductor Circuits

- 14. A circuit consists of one inductor connected to an emf. The peak current through the inductor is 4.0 A. What is the peak current if:
 - a. The peak emf \mathcal{E}_0 is doubled?

$$I_L = 8.0A$$
 since $I_L = \frac{V_L}{X_L} = \frac{\varepsilon_0}{\omega L}$

b. The inductance L is doubled?


c. The frequency ω is doubled?

$$I_{L} = 2.0A$$

- 15. Current and voltage graphs are shown for an inductor circuit with $\omega = 1000$ rad/s.
 - a. What is the inductive reactance X_1 ?


$$X_{L} = \frac{V_{L}}{I_{L}} = \frac{10V}{10 \times 10^{-3} A} = 1000 \Omega$$

b. What is the inductance L?

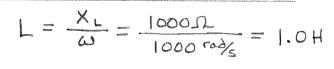


V_L (V) Voltage Current 10

16. Consider these four circuits.

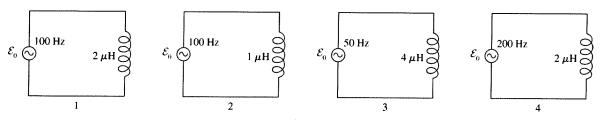

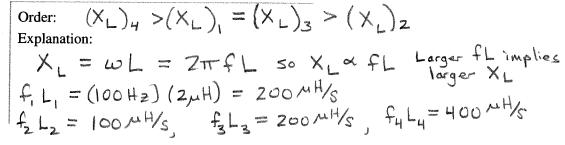Rank in order, from largest to smallest, the inductive reactances $(X_L)_1$ to $(X_L)_4$.



32.5 The Series RLC Circuit

- 17. The resonance frequency of a series RLC circuit is 1000 Hz. What is the resonance frequency if:
 - a. The resistance R is doubled?

b. The inductance L is doubled?

c. The capacitance C is doubled?

d. The peak emf \mathcal{E}_0 is doubled?


e. The frequency ω is doubled?

18. For these combinations of resistance and reactance, is a series *RLC* circuit in resonance (Yes or No)? Does the current lead the emf, lag the emf, or is it in phase with the emf?

R	$X_{ m L}$	$X_{\rm C}$	Resonance?	Current?
100Ω	$100~\Omega$	50 Ω	No.	Lags.
100Ω	50 Ω	100Ω	No.	Leads.
100Ω	75 Ω	75 Ω	Yes.	In phase.

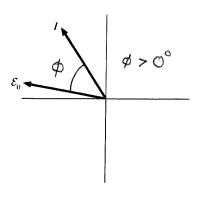
19. In this series *RLC* circuit, is the emf frequency less than, equal to, or greater than the resonance frequency ω_0 ? Explain.

Greater than. Here current lags the emf,
so
$$X_L > X_C$$
. By definition,
 $X_L = \omega L$ and $X_C = \frac{1}{\omega C}$ so
 $\frac{X_L}{X_C} = \omega^2 LC > 1 \implies \omega > \frac{1}{\sqrt{LC}} = \omega_0$



Given $\omega < \omega_0$, then the reactances must have values such that $X_L < X_C$ so the phase angle φ between the emf and the current is less than zero. The current leads the emf.

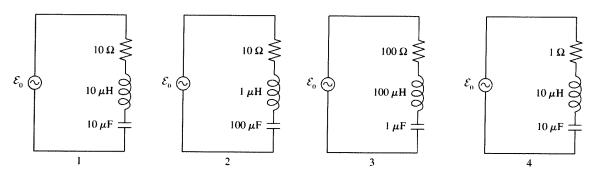21. Consider these four circuits. They all have the same resonance frequency ω_0 .



Rank in order, from largest to smallest, the maximum currents $(I_{\text{max}})_1$ to $(I_{\text{max}})_4$.

Order:
$$(T_{\text{max}})_{\text{H}} > (T_{\text{max}})_{\text{I}} = (T_{\text{max}})_{\text{Z}} > (T_{\text{max}})_{\text{3}}$$

Explanation:
$$(T_{\text{max}}) = \frac{\mathcal{E}_0}{R} = \frac{\mathcal{E}_0}{10\Omega} \qquad (T_{\text{max}})_{\text{I}} = \frac{\mathcal{E}_0}{10\Omega} = (T_{\text{max}})_{\text{I}}$$

$$(T_{\text{max}})_{\text{I}} = \frac{\mathcal{E}_0}{10\Omega} = \frac{(T_{\text{max}})_{\text{I}}}{10} \qquad (T_{\text{max}})_{\text{I}} = \frac{\mathcal{E}_0}{10\Omega} = 10 (T_{\text{max}})_{\text{I}}$$

32.6 Power in AC Circuits

22. The current in a series *RLC* circuit lags the emf by 20°. You cannot change the emf. What two different things could you do to the circuit that would increase the power delivered to the circuit by the emf?

The power will increase when the current increases. To increase current:

- 1) reduce resistance R in the circuit.
- 2) choose L and C components such that their reactances are more closely equal, X_= Xc.

 This will more closely match the frequency of the given emf with the resonant frequency of the circuit.

- 23. An average power dissipated by a resistor in an all-resistor circuit is 4.0 W. What is P_{avg} if:
 - a. The resistance R is doubled?

b. The peak emf \mathcal{E}_0 is doubled?

c. The frequency is doubled?

24. Consider these two circuits.

a. Which has the larger peak current? Or do both have the same peak current? Explain.

The peak current is larger in circuit 2.

Circuit 1:
$$I_{peak} = \frac{\mathcal{E}_0}{2R}$$

Circuit 2: $I_{peak} = \frac{\mathcal{E}_0}{Z} = \frac{\mathcal{E}_0}{\sqrt{R^2 + R^2}} = \frac{\mathcal{E}_0}{\sqrt{Z}R}$

b. Which emf supplies the larger power? Or do both supply the same power?

Both circuits supply the same power.

Circuit 1: Psource =
$$I_{rms} \mathcal{E}_{rms} = \frac{I_{peak}}{\sqrt{2}} \frac{\mathcal{E}_{o}}{\sqrt{2}} = \frac{\mathcal{E}_{o}}{2\sqrt{2}R} \frac{\mathcal{E}_{o}}{\sqrt{2}} = \frac{\mathcal{E}_{o}}{4R}$$

Circuit 2: Psource = $I_{rms} \mathcal{E}_{rms} \cos \phi$

where $\phi = \tan^{-1}(-x_{c}) = -45^{\circ} \cos \cos \phi = \frac{1}{\sqrt{2}}$

Psource = $I_{peak} \mathcal{E}_{o} = \frac{1}{\sqrt{2}} \frac{\mathcal{E}_{o}}{\sqrt{2}} = \frac{\mathcal{E}_{o}}{4R}$